

Report for Experiment 6

Name THOMAS CROW
Date 10-18-2001
Class EE 710

ABSTRACT:

DATA:

$$I_T = \frac{V_s}{R_T} = \frac{15V}{4.995k\Omega} =$$

Table 6-1

Component	Listed Value	Measured Value
R_1	1.0 k Ω	0.989 k Ω
R_2	1.5 k Ω	1.492 k Ω
R_3	2.2 k Ω	2.171 k Ω
R_4	330 Ω	0.328 k Ω
R_T	4.98 k Ω	4.995 k Ω

Table 6-2

	Computed Value	Measured Value
I_T	3.003 mA	2.996 mA
V_{AB}	3.003 V	2.997 V
V_{BC}	4.505 V	4.510 V
V_{CD}	6.607 V	6.548 V
V_{DE}	0.991 V	0.984 V

$V_{AB} = I \cdot R_1 =$
 $3.003 \text{ mA} \cdot 1 \text{ k}\Omega =$
 3.003 V
 $V_{BC} = I \cdot R_2 =$
 $3.003 \text{ mA} \cdot 1.5 \text{ k}\Omega =$
 4.505 V
 $V_{CD} = I \cdot R_3 =$
 $3.003 \text{ mA} \cdot 2.2 \text{ k}\Omega =$
 6.607 V
 $V_{DE} = I \cdot R_4 =$
 $3.003 \text{ mA} \cdot 330 \Omega =$
 0.991 V

Table 6-3

Step Number	Kirchhoff's Voltage Law (Measured Values)
7	$15V - 2.997 - 4.510 - 6.548 - 0.984 =$
8	$6.548 + 4.510 - 2.997 - 15 + 0.984 =$
9	$0 - 0 - 0 - 0 = 0$

$-0.039 \text{ V} \quad 0.26\%$
 -0.039 V

RESULTS AND CONCLUSION:

FURTHER INVESTIGATION RESULTS:

APPLICATION PROBLEM RESULTS:

EVALUATION AND REVIEW QUESTIONS:

1. Why doesn't the starting point for summing the voltages around a closed loop make any difference?

PER KIRCHHOFF'S VOLTAGE LAW, ALL VOLTAGE RISES AND DROPS IS EQUAL TO ZERO

2. Kirchhoff's voltage law applies to any closed path, even one without current. How did the result of step 9 show that this is true?

Without current, the voltages across the circuit dropped to zero.

3. Based on the result you observed in step 9, what voltage would you expect in a 120 V circuit across an open (blown) fuse?

ZERO

4. Use Kirchhoff's voltage law to find V_x in Figure 6-7.

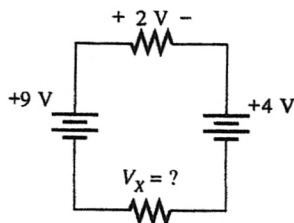


Figure 6-7

$$9 - 2 + 4 - V_x = 0$$

$$V_x = 11V$$

5. A $10\ \Omega$ resistor is in series with a bulb and a 12 V source.

- (a) If 8 V is across the bulb, what voltage is across the resistor? 4V
- (b) What is the current in the circuit? 0.4A
- (c) What is the resistance of the bulb? 20Ω

$$I = \frac{4V}{10\Omega} = 0.4A$$

$$R_T = \frac{12V}{0.4A} = 30\Omega$$

$$30\Omega - 10\Omega = 20\Omega$$

6. A student wishes to limit the current to an LED (light-emitting diode) to 10.0 mA. The source voltage is +5 V and the diode drops 1.8 V.

- (a) What value resistance is required? 320Ω
- (b) What power is dissipated in the resistor? 32mW

$$5 - 1.8V = 3.2V$$

$$R_R = \frac{3.2V}{10mA} = 320\Omega$$

$$10mA \cdot 3.2V =$$